



# EL 653

## Diseño CMOS




# Metodologia General

- CMOS produce funciones invertidas
- Metodo
  - Invierta la función en caso que sea necesario
  - Diseñe la función NMOS (pull down) (AND/OR → serie/paralelo)
  - Diseñe el circuito dual PMOS (pull up) (AND/OR → paralelo/serie)



# Metodologia General

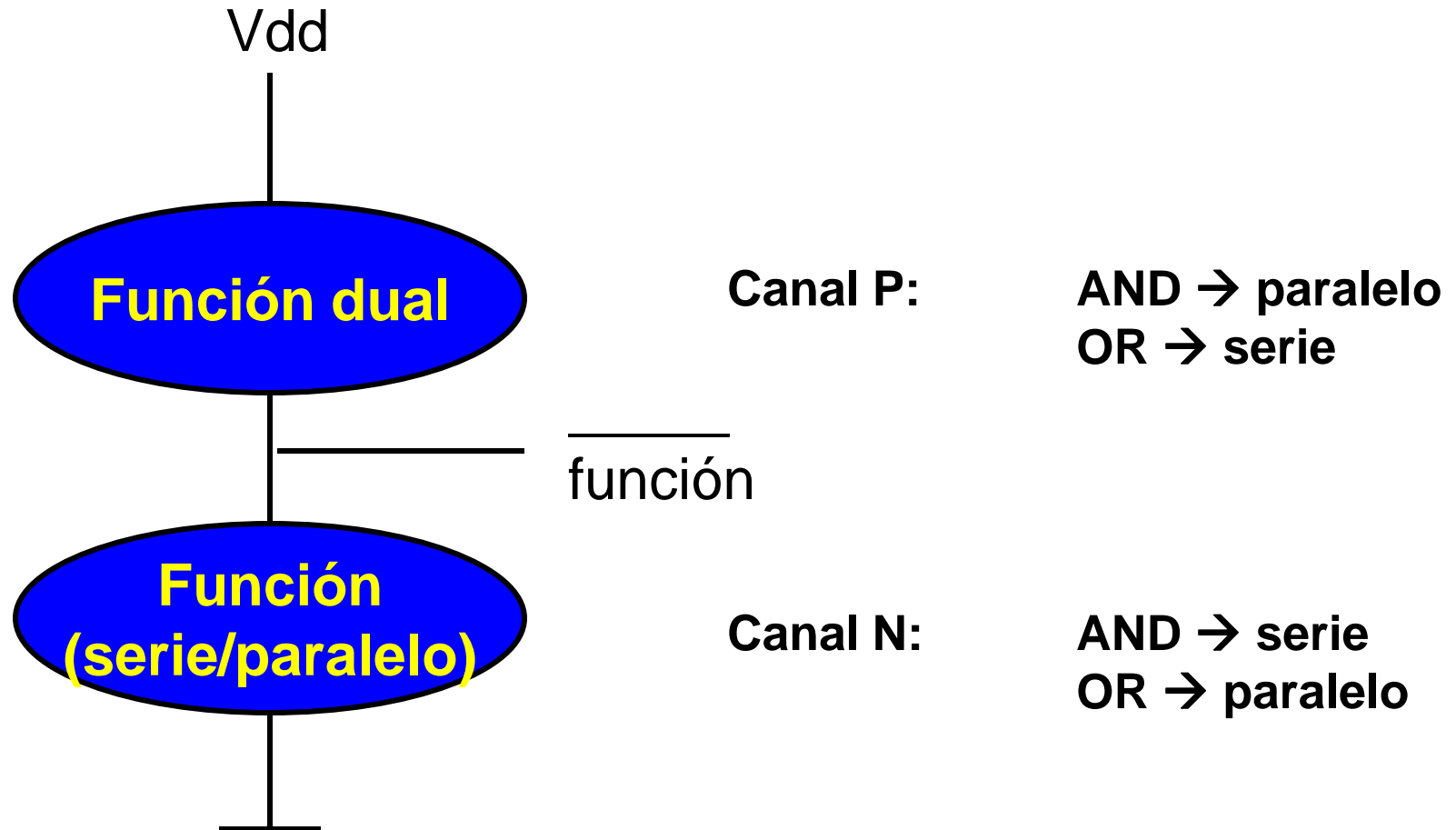



# Ejemplo 1

$$f = \overline{a \cdot b + c}$$


N – channel (pull down)

Formato:  $\overline{(ANDs, Ors)}$

$$f = \overline{a \cdot b + c}$$

( a AND b) OR C


( a serie b) paralelo C

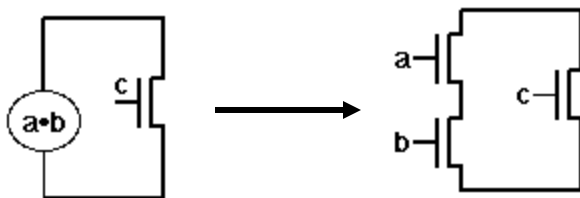

P – channel (pull up)


Formato dual: ( a AND b) OR C

( a paralelo b) serie C

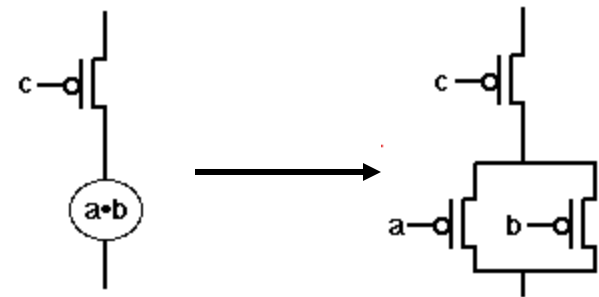







# Ejemplo 1 - Layout

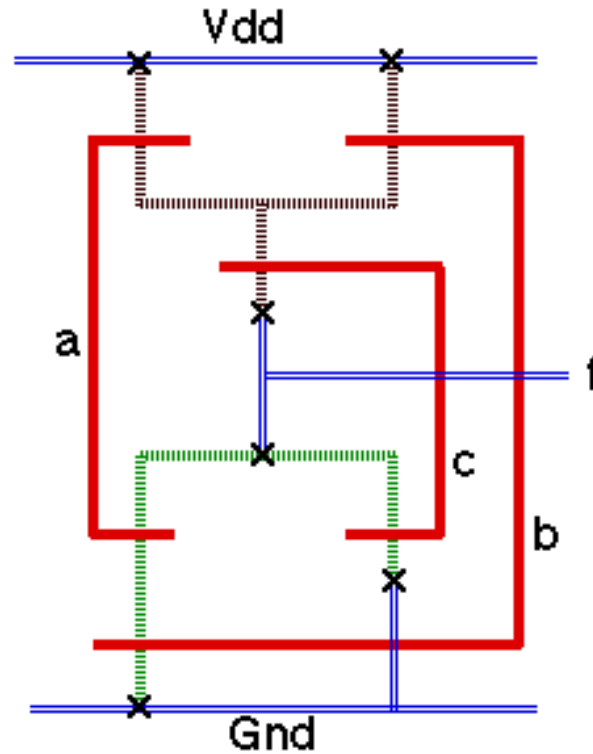



$$f = [a (b + c)] + (d \bullet e)$$

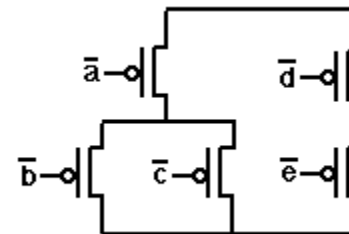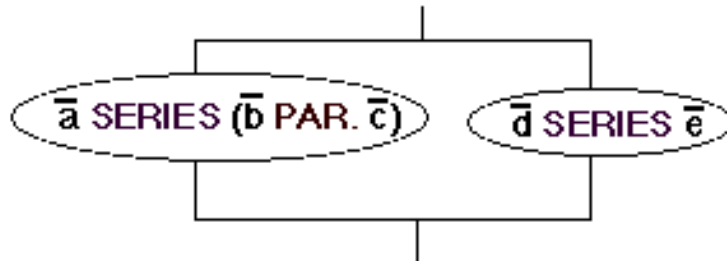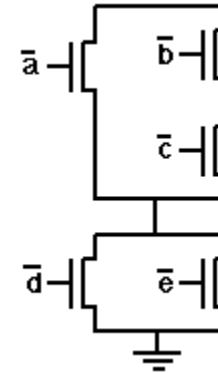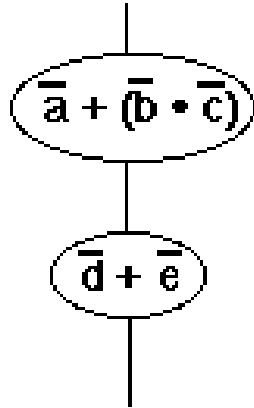



$$f = [a (b + c)] + (d \bullet e)$$

